Digital Electronies (Diplome Only) 2004

plogl SWM

(a) De Morgan's theorem: $a.\overline{b} = \overline{a} + \overline{b}$ $\overline{a+b} = \overline{a}.\overline{b}$

$$\overline{a.b} = \overline{a} + \overline{b}$$

$$\overline{a+b} = \overline{a}$$
. E

Context: Boolean algebra (ledwe2)

Logic minimisation (lecture 3)

(b) A mintern of a Boolean variables is the conjuction of all variables in either Their complemented or uncomplemented from

A prime implicant is a term which cannot be further combined. An essential from is a prime implicant that no other which covers a mintern that no other prime implicant covers.

(c) K-map for f=(a.b) \$\mathcal{D}\$ (c+d):

	•	a	<u>D</u>		
	0	0		0	
c	M		0	1	_
	Ø	X	0	XI	_
a -	V	IJ	Ó	V	

 $f = \overline{a}.c + \overline{b}.c + \overline{a}.d + \overline{b}.d + ab\overline{c}\overline{d}$ All terms are gime & essential terms

(d) K-may for fabore with don't cares for a.b

	<u>a _b</u>				
	Ü	0	χ	O	
	1	1	X	1	
d	A	I	X	K	
	U		Χ	IJ	

fis now = c + d