 


Solution A

Pulls up when $A=1$ & $B=0$ or when $A=0$ & $B=1$. Pulls down when $A=B=0$ or when $A=B=1$.

Each input is controlling four transistors which imposes a heavy load.

Using nFET pull-ups and pFET pull-downs restricts the voltage swing on the output, which will be exacerbated when gates are cascaded.



Invertors buffer inputs and allow pFET pull-ups and nFET pull-downs.

Use two invertors on each of three inputs, pull up on $AB'C'$, $A'BC'$, $A'B'C$ and ABC , pull down on $A'B'C'$, $A'BC$, $AB'C$ and ABC' . Revised circuit uses 16 transistors so cascaded pair uses 32 and suffers 6 gate delays. Complex circuit uses 36 transistors but only suffers 3 gate delays.

Use an extended C element for each of Q_0 and Q_1 . Preliminary circuit has A_0 , A_1 , B_0 & B_1 feeding pFETs in series for pull-up and two parallel pull-downs; one with A_0 & B_1 feeding nFETs in series, the other with A_1 & B_0 . This drives invertor to give Q_1 with weak feed-back invertor to hold state.

The question relates to the CMOS design part of the course. The last part expects knowledge of self-timed circuit design.