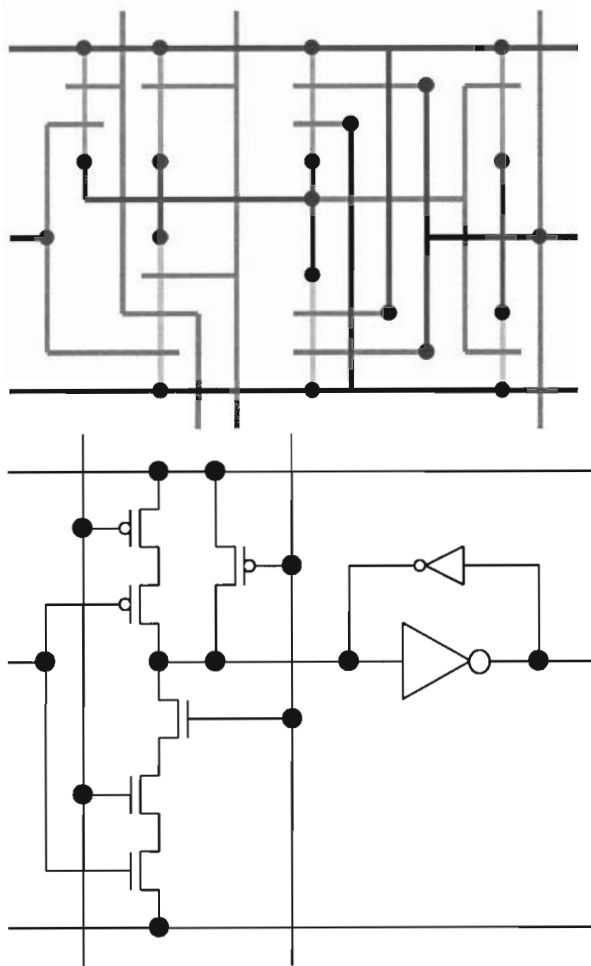


p7q2  
PR

VLSI

2000

Answer



C element with external reset. Note use of long, turned-on transistors to attenuate weak feed-back.