

(a) The minimum sum of products can easily identified from the table:


$$S_0 = EN \cdot \bar{A}_1 \cdot \bar{A}_0$$

$$S_1 = EN \cdot \bar{A}_1 \cdot A_0$$


$$S_2 = EN \cdot A_1 \cdot \bar{A}_0$$

$$S_3 = EN \cdot A_1 \cdot A_0$$

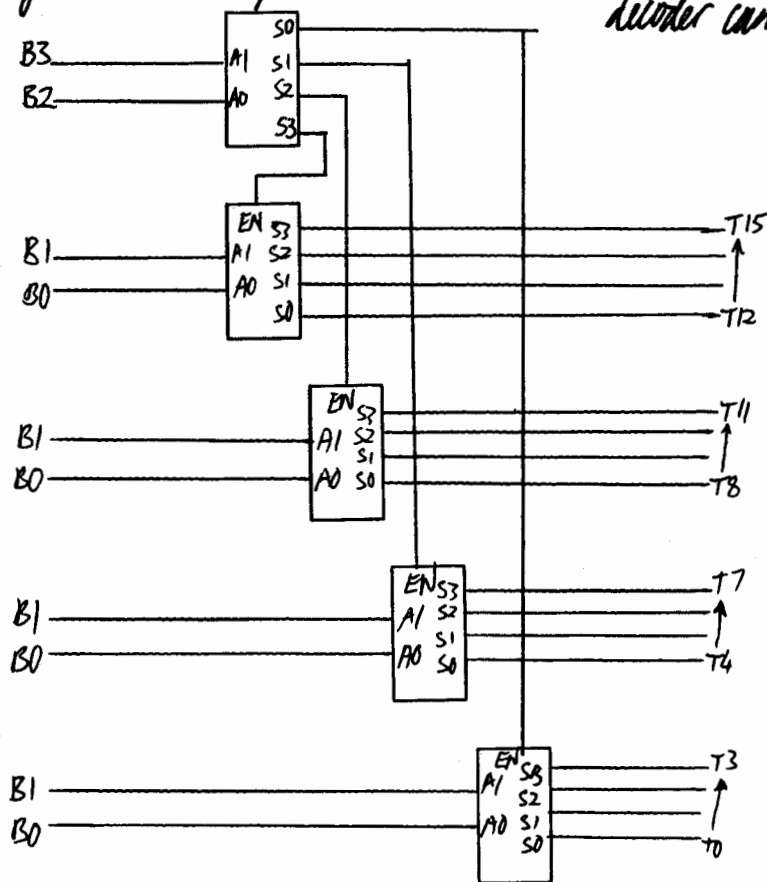(b) Assuming the selector inputs are $B_0 \rightarrow B_3$ & the outputs are $T_0 \rightarrow T_{15}$ a 4 \rightarrow 16 line decoder can be constructed as follows:



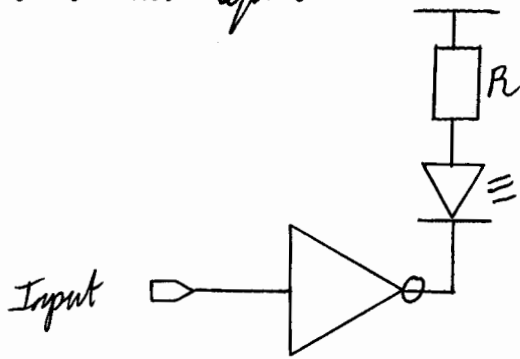(c) The circuit required to drive the LED is:



If the supply voltage is 5V, the output is 0V & the drop across the LED is 1.5V the drop across R will be 3.5V.

The max. current is 20mA. $V=IR$ so $R = \frac{V}{I} = \frac{3.5}{20 \times 10^{-3}} = 175 \Omega$

(d)

