

Digital Electronics Paper 2 Question 2 2005

Also for Diploma & Part II (gen) Paper 11 Question 1

(a) The state table for the 0→5 counter is:

current state			next state		
C	B	A	C'	B'	A'
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	X	X	X
1	1	1	X	X	X

Computer Science Tripos Part II (General) 2005

Paper 11 Question 1

SWM — Digital Electronics

by inspection, $A' = \bar{A}$

for B'

	A	B
C	0	1
	0	0
	1	0
	1	1


for C'

	A	B
C	0	1
	0	0
	1	0
	1	1

so $B' = (A \oplus B) \cdot \bar{C}$
 min. sum of products for B' :
 $B' = A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B$


$$C' = A \cdot B + \bar{A} \cdot C$$

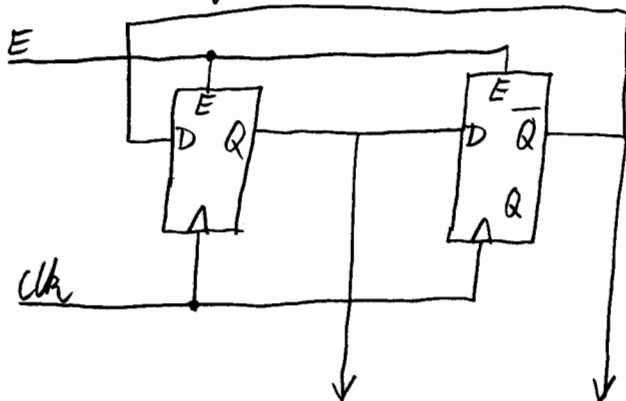(b) This is basically from the notes but many will have to derive the circuit.



P2Q2 2005 cont...

(c)

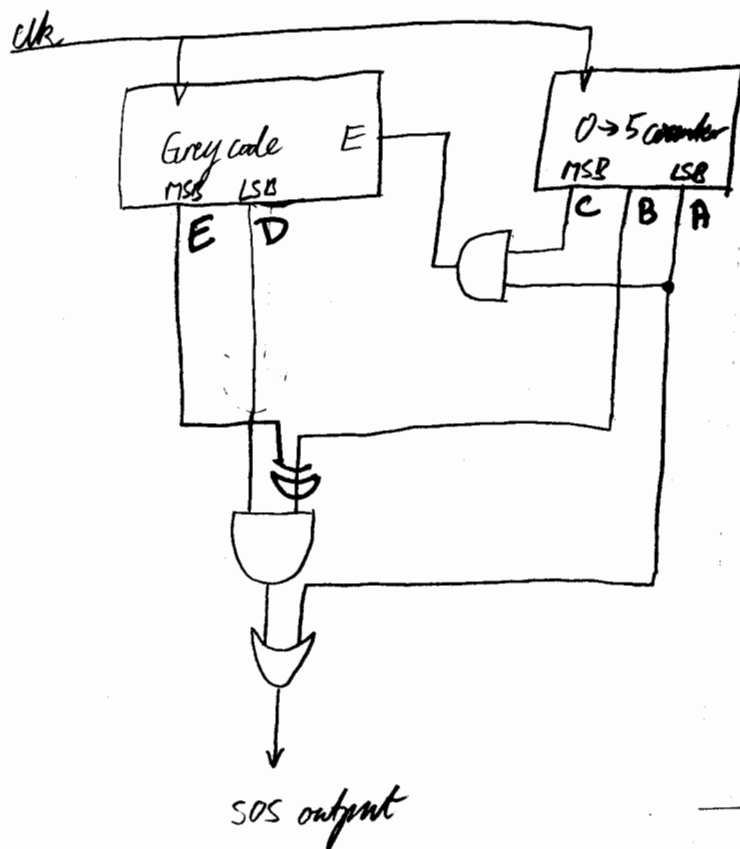

sos output = 1 when A=1

when A=0, sos output =

		B		C
D	E	0	0	X
		0	1	X
E	D	1	0	X
		0	0	X

$$= \bar{B}DE + BDE$$

$$= D(B \oplus E)$$

$$\therefore \text{sos output} = A + D(B \oplus E)$$

This question covers lecture 3 (logic minimisation), 5 (flip-flops) and 6 & 7 (state machines).