 


Question B

Give transistor level designs for 2-input NAND gates using static and dynamic CMOS, explaining how the latter is controlled by a clock. [10 marks]


Comment on the relative merits of the two methods for evaluating more complicated combinatorial functions, including transistor count, wiring complexity, speed and implications for cascaded logic. [5 marks]

Consider the following circuit for a set-reset latch in a form of Domino logic:



Explain its operation and specify carefully the sense of the input and output signals. [5 marks]

Answer

 

Dynamic logic precharges when the clock, c , is low and evaluates when it is high.

Replace the two transistors implementing the AND function by an arbitrary piece of combinational logic. For n inputs, static uses $2n$ transistors and dynamic $n+2$ with simpler wiring. Dynamic logic is generally faster, but the output is only available when c is high. The dynamic version has problems with an internal race when gates are cascaded, requiring the use of Domino or Nora logic.

When c is low, the output is reset low. When c is high, raising d sets the output high. The inverter and two additional transistors provide weak feed-back to retain the state.